



Alexandria Higher Institute of Engineering & Technology (AIET)

Communications & Mechatronic Departments	2011/2012	Second Year
EME 231 & EME 233	Electromechanical Energy Conversion Transformers & Machines	Mid of-Semester Exam 2, Date 18 / 12 / 2011
Examiners:	Prof. Dr. Kamel Mohamed Soliman	Time: 1 hour

**Question one: (1 mark)**

State briefly one application for one – to – one ratio transformer.

**Question two: (1 mark)**

For transformer of primary side P and secondary side S , what is wrong in this equation? Why ?

$$V1 \setminus V2 = I2 \setminus I1 = P1 \setminus P2 = \text{transformation ratio}$$

**Question three: (2 marks)**

Why constant current transformer must operate at saturation region .

**Question four: (6 marks)**

Tests are performed on a single phase 10 KVA , 2200 / 220 volt, 60 Hz transformer, and the following results are obtained :

	Open circuit test	Short circuit test
V	220V	150V
I	2.5A	4.55A
P	100watt	215watt

1-Derive the parameters for the approximate equivalent circuit referred to the high voltage side

2-Determine the Power Factor for the no-load and short circuit tests

3-Determine the voltage regulation in percent for the case of 0.75 full load , 0.6 power factor lagging

"الإجابة المختصرة والمدعمة بالرسم أفضل"  
"الإجابة بأي لغة"  
( جزء من الدرجة على صحة أرقام الجواب النهائي )


Second Mid-Term-Solution

①

1] a- application of one-to-one ratio trf:

- separating AC from superimposed

DC component

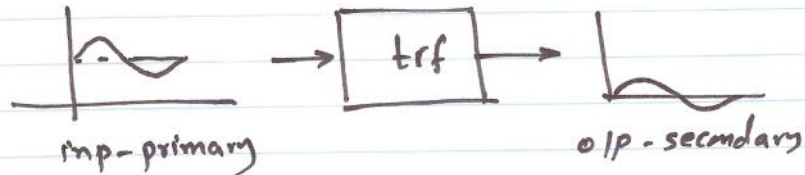

b-  $\frac{P_1}{P_2} \neq a$  because  $P_1 \cong P_2$

c- constant current trf. depends mainly on

- The repulsion and attraction forces

produced from the variable leakage

flux linking from one coil to the

other one.

- This leakage is changed mainly due

to saturation

2


a) O.C.T

2

$$P_{oc} = \frac{V_L^2}{R_{cl}}$$

$$\therefore R_{cl} = \frac{V_L^2}{P_{oc}}$$
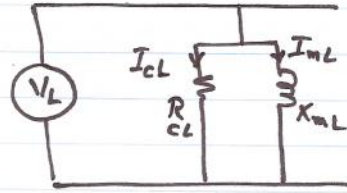
$$= \frac{(220)^2}{100} = \boxed{484 \Omega = R_{cl}}$$



$$I_{cl} = \frac{V_L}{R_{cl}} = \frac{220}{484} = \underline{0.45 \text{ A}}$$

$$I_{ml} = \sqrt{I_p^2 - I_{cl}^2} = \sqrt{(7.5)^2 - (0.45)^2} = \underline{2.46}$$

$$\therefore X_{ml} = \frac{V_L}{I_{ml}} = \frac{220}{2.46} = \boxed{89.4 = X_{ml}}$$

$$a = \frac{2200}{220} = 10$$


$$\therefore R_{ch} = a^2 R_L = 100 \times 484 = \boxed{48400 \Omega = R_{ch}}$$

$$X_{mh} = a^2 X_{ml} = 100 \times 89.4 = \boxed{8940 = X_{mh}}$$

S.C.T

③

$$P_{sc} = I_h^2 R_{eqh}$$

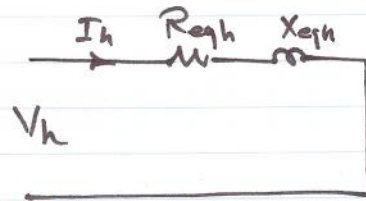


$$\therefore R_{eqh} = \frac{215}{(4.55)^2} = \boxed{10.4 \Omega = R_{eqh}}$$

$$Z_{eqh} = \frac{V_h}{I_h} = \frac{150}{4.55} = \underline{\underline{32.97 \Omega}}$$

$$X_{eqh} = \sqrt{Z_{eqh}^2 - R_{eqh}^2} = \sqrt{(32.97)^2 - (10.4)^2} \\ = \boxed{31.3 \Omega = X_{eqh}}$$

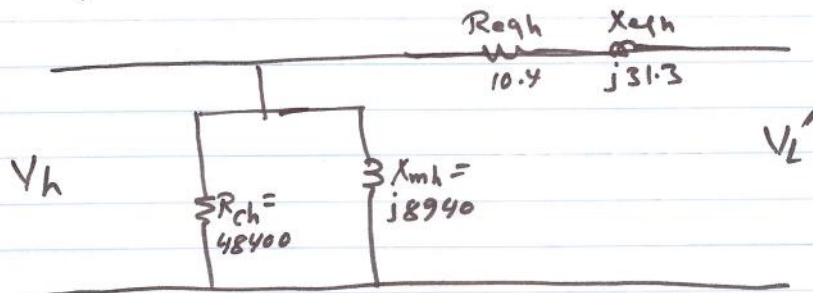$\therefore$  eq<sup>t</sup> circuit- referred to high. v. side is



(b) op. ct. power factor :

$$P = VI \cos \phi$$

$$\cos \phi_{oc} = \frac{100}{220 \times 7.5} = 0.182$$

s.c. p.f. :

$$\cos \phi_{sh.c.} = \frac{215}{150 \times 4.55} = 0.315$$

(3)


© at 75% f.L; 0.6 Lagging P.f :

$$V_{fLh} = \left( \frac{VA}{I} \right)_h = \frac{10000}{2200} = \underline{\underline{4.55 \text{ A}}}$$

$$\therefore I_h = .75 I_{fLh} = .75 \times 4.55$$

$$\boxed{I_h = 3.41 \text{ A} \angle -53.13} \quad (\text{P.f } 0.6 \text{ Lag})$$

=  $I_L'$  referred to primary

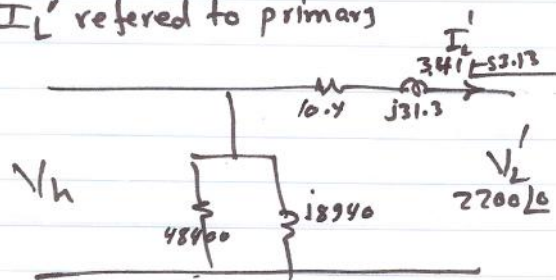

$$V_h = V_L' + I_L' Z_{eph}$$

$$= 2200 \angle 0 + 3.41 \angle -53.13 \times (10.4 + j31.3)$$

$$\boxed{V_h = 2306.94 \angle 0.9}$$

$$VR\% = \frac{V_h - V_L'}{V_L'} \times 100 = \frac{2306.94 - 2200}{2200} \times 100$$

$$\boxed{VR\% = 4.86\%}$$